

# Electricity

---

## Electricity

$Q = It$ , so current = rate of flow of charge

$W = QV$ , so potential difference is the energy per unit charge

$V = IR$ , for an Ohmic conductor  $I \propto V$

A shallower gradient on I-V graph = increased resistance

- An Ohmic conductor as a straight line I-V graph
  - A silicon diode conducts no current until  $V \approx 0.7$  V, after which current flows with very little resistance
  - A filament bulb gives an S-curve: greater resistance at higher voltages as the filament heats up due to increased current flow.
  - The unknown-resistor circuit consists of a variable resistor in series with the unknown resistance, an ammeter and a voltmeter in parallel with the unknown resistance. It can be used to determine the resistance of the unknown resistor.
- 

## Resistivity

resistivity,  $\rho l = RA$  unit:  $\Omega$  m

Superconductors have a resistivity of  $0 \Omega$  m. These are certain materials, which must be cooled below a "transition temperature".

Uses include power transmission lines, strong electromagnets, and very high speed electronic systems.

---

## Power

$$P = \frac{E}{t} = IV = \frac{V^2}{R} = I^2R$$
$$E = VIt$$

---

## EMF and internal resistance

The internal resistance of a cell can be imagined much like a resistor in series with the cell.

$$\text{Electromotive force, } \mathcal{E} = \frac{\text{energy, } E}{Q} = I(R + r) = \text{terminal pd} + \text{lost volts}$$

It is helpful to have awareness of potential dividers and resistive input transducers in this section.